

PROBLEMS:

P.13.1 How many electrons pass through an electric bulb in one minute if 300 mA current is passing through it?

DATA: Charge on an electron = $e = 1.6 \times 10^{-19} \text{ C}$

$$\text{Time} = t = 1 \text{ min} = 60 \text{ s}$$

$$\text{Current} = I = 300 \text{ mA} = 300 \times 10^{-3} \text{ A} = 0.3 \text{ A}$$

$$\text{Number of electrons} = N = ?$$

Sol. As $I = \frac{Q}{t} = \frac{N \times e}{t}$

$$\text{or } N = \frac{I \times t}{e} = \frac{0.3 \text{ A} \times 60 \text{ s}}{1.6 \times 10^{-19} \text{ C}} = \boxed{1.125 \times 10^{20}}$$

P.13.2 A charge of 90 C passes through a wire in 1 hour and 15 minutes. What is the current in the wire?

DATA: charge = $Q = 90 \text{ C}$

$$\text{Time} = t = 1 \text{ hr } 15 \text{ min} = 4500 \text{ s}$$

$$\text{current} = I = ?$$

Sol. As $I = \frac{Q}{t} = \frac{90 \text{ C}}{4500 \text{ s}} = 0.02 \text{ A} = 0.02 \times 10^{-3} \times 10^3 \text{ A}$

$$I = 20 \times 10^{-3} \text{ A} = \boxed{20 \text{ mA}}$$

P.13.2 Find the equivalent resistance of the circuit in the fig, total current drawn from the source and the current through each resistor.

(P.T.O)

Sol. R_1 and R_2 are connected in parallel between points A and B

$$\text{then } \frac{1}{R_A} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{6} + \frac{1}{6} = \frac{1}{3}$$

$$\therefore R_A = 3\Omega \quad \text{--- (1)}$$

Now R_A and R_3 are in series. The equivalent resistance

R_e is given by

$$R_e = R_A + R_3 = 3 + 3 = 6\Omega \quad \text{--- (2)}$$

$$\text{Current} = I = \frac{V}{R_e} = \frac{6V}{6\Omega} = 1.0A \quad \text{--- (3)}$$

current through R_1

$$I_1 = \frac{V_{AB}}{R_1}$$




$$I_1 = \frac{3\text{volts}}{6\Omega} = 0.5A \quad \text{--- (4)}$$

current through R_2

$$I_2 = \frac{V_{AB}}{R_2} = \frac{3V}{6\Omega} = 0.5A \quad \text{--- (5)}$$

current through R_3
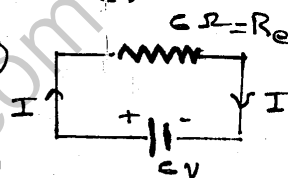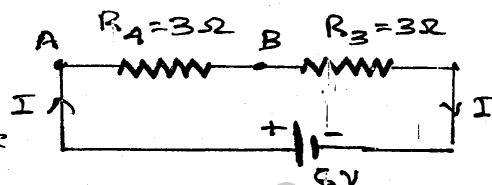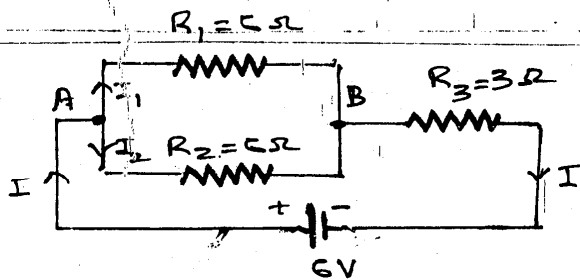
$$I = I_1 + I_2 = 1.0A \quad \text{--- (6)}$$



P.13.4 A rectangular bar of iron is 2.0 cm by 2.0 cm in cross section and 40 cm long. Calculate its resistance if the resistivity of iron is $11 \times 10^{-8} \Omega \times m$.

DATA. Area of bar = $A = 2\text{cm} \times 2\text{cm} = 4\text{cm}^2 = 4 \times 10^{-4} \text{m}^2$

Length of bar = $L = 40\text{cm} = 0.4\text{m}$

Resistivity of bar = $\rho = 11 \times 10^{-8} \Omega \times m$

Resistance = $R = ?$

Sol. As $R = \frac{\rho L}{A} = \frac{11 \times 10^{-8} \Omega \times m \times 0.4\text{m}}{4 \times 10^{-4} \text{m}^2} = 1.1 \times 10^{-4} \Omega$

P.13.5 The resistance of an iron wire at 0°C is $1 \times 10^{-4} \Omega$.

What is the resistance at 500°C if the temp. co-efficient of resistance of iron is $5.2 \times 10^{-3} \text{K}^{-1}$?

DATA: Resistance at $0^\circ\text{C} = R_0 = 1 \times 10^{-4} \Omega$

Resistance at $500^\circ\text{C} = R_t = ?$

$$\alpha = 5.2 \times 10^{-3} \text{K}^{-1}$$

$$\text{change in temp. } t = (T - 0^\circ) = (500 + 273) - 273 = 500 \text{K}$$

Sol. As $\alpha = \frac{R_t - R_0}{R_0 \times t}$

$$5.2 \times 10^{-3} \text{K}^{-1} = \frac{R_t - 1 \times 10^{-4}}{1 \times 10^{-4} \times 500}$$

$$R_t = \boxed{3.6 \times 10^{-4} \Omega}$$

P.13.6 calculate terminal P.d of each of cells in the given circuit.

Sol. The circuit consists of two batteries. The total voltage in the circuit is

$$V = E_1 - E_2 = 24 - 6 = 18 \text{ volts} \quad \text{--- (1)}$$

Total resistance of the circuit $= r_1 + R + r_2$

$$R = 0.1 + 8 + 0.9 = 9 \Omega \quad \text{--- (2)}$$

current flowing through the loop $= I = \frac{V}{R} = \frac{18 \text{V}}{9 \Omega} = 2 \text{A} \quad \text{--- (3)}$

For battery E_1

$$V_1 = E_1 - I \times r_1 = 24 - 2 \times 0.1 = \boxed{23.8 \text{ volts}}$$

Where ' V_1 ' is the terminal P.d of battery E_1 .

For battery E_2

$$V_2 = E_2 + I \times r_2 = 6 + 2 \times 0.9 = \boxed{7.8 \text{ volts}}$$


Where ' V_2 ' is the terminal P.d of battery E_2 .

This is the case when battery is being charged.

(P.T.O)

P.13.7 Find the current which flows in all the resistances of the circuit.

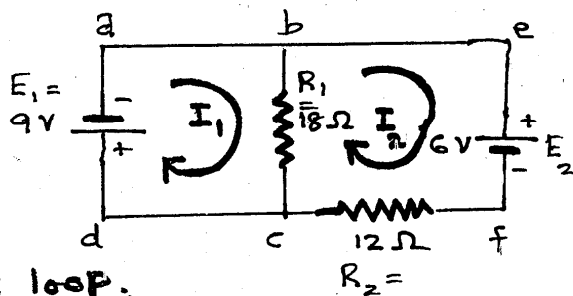Sol. Let current I_1 is following in the left loop and current I_2 is flowing in the right loop. Now, using Kirchhoff's rule for the left loop.



$$-(I_1 - I_2) \times 18 + 9 = 0$$

$$(I_1 - I_2) \times 18 = 9$$

$$I_1 - I_2 = \frac{9}{18} = 0.5 \text{ A}$$

or $I_1 = I_2 + 0.5$ ——— ①

Using Kirchhoff's rule for the right loop.

$$-(I_2 - I_1) \times 18 - 12I_2 - 6 = 0$$

$$-18I_2 + 18I_1 - 12I_2 = 6 \text{ volt}$$

$$-30I_2 + 18I_1 = 6$$

$$-5I_2 + 3I_1 = 1$$
 ——— ②

Putting value of I_1 from eq. ① into eq. ②, we have;

$$-5I_2 + 3(I_2 + 0.5) = 1$$

$$-5I_2 + 3I_2 + 1.5 = 1$$

$$-2I_2 = -0.5$$

$$I_2 = \frac{0.5}{2} = 0.25 \text{ A}$$
 ——— ③

Substituting the value of I_2 in eq. ①, we have

$$I_1 = 0.25 + 0.5 = 0.75 \text{ A}$$
 ——— ④

Now,

$$\text{current through } 18 \Omega \text{ resistance} = I_1 - I_2$$

$$I = 0.75 - 0.25$$

$$= 0.5 \text{ A}$$

$$\text{current through } 12 \Omega \text{ resistance} = I_2 = 0.25 \text{ A}$$

(P.T.O)

P. 13.8. Find the current and power dissipated in each resistance of the circuit as shown.

Sol.


Let I_1 (Anticlockwise)

be the current flowing through loop 1 and

I_2 (Anticlockwise) be

the current flowing

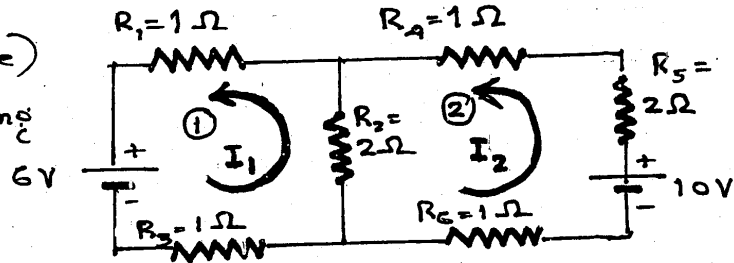through loop 2. Applying Kirchhoff's second rule to solve this circuit.



For loop 1

$$-6 - 1 \times I_1 - 2(I_1 - I_2) - 1 \times I_1 = 0$$

$$-4I_1 + 2I_2 = +6$$

$$\text{or } -2I_1 + I_2 = +3 \quad \text{--- (1)}$$

For loop 2

$$+10 - 1 \times I_2 - 2(I_2 - I_1) - 1 \times I_2 - 2 \times I_2 = 0$$

$$+2I_1 - 6I_2 = -10 \quad \text{--- (2)}$$

Adding eqs. (1) and (2), we have

$$-5I_2 = -7$$

$$I_2 = \frac{7}{5} = 1.4 \text{ A} \quad \text{--- (3)}$$

Putting this value of I_2 in eq. (1), we have

$$-2I_1 + 1.4 = +3$$

$$2I_1 = -3 + 1.4$$

$$I_1 = \frac{-1.6}{2} = -0.8 \text{ A} \quad \text{--- (4)}$$

The negative sign with I_1 shows that actually it is flowing through the loop in clockwise direction


$$\therefore I_1 = 0.8 \text{ A} \quad \text{and} \quad I_2 = 1.4 \text{ A}$$

current through R_1 and $R_3 = I_1 = 0.8 \text{ A}$

current through R_2

$$= I_1 + I_2 = 1.4 + 0.8 = 2.2 \text{ A}$$

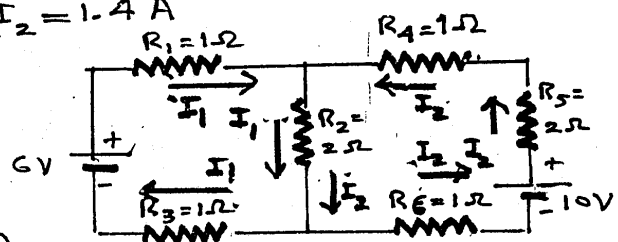current through R_4, R_5 & $R_6 = I_2 = 1.4 \text{ A}$



(P.T.O)

13.40

Power dissipation.

$$\text{Power dissipated in } R_1 = I_1^2 R_1$$

$$\therefore P_1 = (0.8)^2 \times 1 = 0.64 \text{ watt.}$$

$$\text{Power dissipated in } R_3 = I_1^2 R_3$$

$$\therefore P_3 = (0.8)^2 \times 1 = 0.64 \text{ watt.}$$

$$\text{Power dissipated in } R_2 = (I_1 + I_2)^2 R_2$$

$$\therefore P_2 = (2.2)^2 \times 2 = 9.68 \text{ watt.}$$

$$\text{Power dissipated in } R_4 = I_2^2 R_4 =$$

$$\therefore P_4 = (1.4)^2 \times 1 = 1.96 \text{ watt.}$$

$$\text{Power dissipated in } R_6 = I_2^2 R_6$$

$$\therefore P_6 = (1.4)^2 \times 1 = 1.96 \text{ watt}$$

$$\text{Power dissipated in } R_5 = I_2^2 R_5$$

$$\therefore P_5 = (1.4)^2 \times 2 = 3.92 \text{ watt.}$$