

PROBLEMSP.18.1

DATA. $I_B = 100 \mu A = 100 \times 10^{-6} = 10^{-4} A$

$$\beta = 100$$

- (i) current flowing through collector = $I_C = ?$
 (ii) current flowing through emitter = $I_E = ?$
 (iii) $I_C / I_B = ?$

Sol. (i) As $\frac{I_C}{I_B} = \beta = 100$

$$I_C = 100 I_B = 100 \times 10^{-4} = 10^{-2} A = \boxed{10 \text{ mA}}$$

(ii) $I_E = I_C + I_B$
 $= 10^{-2} + 10^{-4} = 10^{-2} (1 + 0.01) A$
 $= 10^{-2} (1.01) A = 10^{-2} (1.01) \times 10^3 \text{ mA}$
 $= 10 (1.01) = \boxed{10.01 \text{ mA}}$

(iii) $\frac{I_C}{I_E} = \frac{10 \text{ mA}}{10.01 \text{ mA}} = \boxed{0.999}$

P.18.2

DATA: $I_c = 10 \text{ mA} = 10^{-2} \text{ A}$ = collector current
 current gain = $\beta = 200$
 Base emitter voltage = $V_{BE} = 0.6 \text{ V}$
 $V_{CC} = 9 \text{ V}$
 $R_B = ?$

sol. As $\beta = I_c / I_B$
 $I_B = \frac{I_c}{\beta} = \frac{10^{-2}}{200} = 0.5 \times 10^{-4} \text{ A}$ — (1)

We know that

$$V = V_{CC} - V_{BE}$$
 — (2)

$$V = 9 - 0.6 = 8.4 \text{ volt}$$
 — (3)

Using the relation;

$$V = I_B R_B$$

$$R_B = \frac{V}{I_B} = \frac{8.4}{0.5 \times 10^{-4}} = 16.8 \times 10^4 \Omega$$

$$R_B = \boxed{168 \text{ K}\Omega}$$

P.18.3.

DATA: $V_{CC} = 9 \text{ V}$
 $V_{CE} = 7.875 \text{ V}$
 $R_c = 1 \text{ K}\Omega = 10^3 \Omega$
 $R_B = 100 \text{ K}\Omega = 10^5 \Omega$
 $\beta = 100$

(i) Base current = $I_B = ?$

(ii) collector current = $I_c = ?$

(iii) Potential drop across $R_c = V_c = ?$

sol. Potential drop across $R_c = V_{CC} - V_{CE}$

(ii) $\therefore I_c = \frac{V_{CC} - V_{CE}}{R_c} = \frac{1.125}{10^3} = 1.125 \times 10^{-3} \text{ A} = \boxed{1.125 \text{ mA}}$ — (1)

(i) put $\beta = \frac{I_c}{I_B}$

$$\text{or } I_B = \frac{I_c}{\beta} = \frac{1.125 \times 10^{-3} \text{ A}}{100} = 11.25 \times 10^{-6} \text{ A}$$

$$I_B = \boxed{11.25 \mu\text{A}}$$

(P.T.O)

As
 (iii) Potential drop across $R_c = \boxed{1.125 \text{ V}}$
 OR Potential drop across $R_c = I_c R_c$
 $= 1.125 \times 10^{-3} \times 10^3$
 $= \boxed{1.125 \text{ V}}$

P.18.4 :

DATA : $R_1 = 10 \text{ K}\Omega = 10 \times 10^3 \Omega$
 $R_2 = 4 \text{ K}\Omega = 4 \times 10^3 \Omega$

output of op-amp circuit = $V_o = ?$

Sol. Using Kirchoff's law
 (current through R_1) + (current through R_2) = (current through R_3)

$$I_1 = \text{Current through } R_1 = \frac{(5 - 0) \text{ V}}{10 \times 10^3} = 0.5 \times 10^{-3} \text{ A} \quad \text{--- (1)}$$

$$I_2 = \text{Current through } R_2 = \frac{-2 \text{ V} - 0}{4 \times 10^3} = -0.5 \times 10^{-3} \text{ A} \quad \text{--- (2)}$$

$$I = \text{Total current through } R_3 = I_1 + I_2$$

$$= 0.5 \times 10^{-3} - 0.5 \times 10^{-3} = 0$$

$$\therefore V_o = \text{output} = \boxed{0} \quad \therefore I = \frac{V_o - 0}{R_3} = \frac{V_o}{20 \times 10^3}$$

$$0 = \frac{V_o}{20 \times 10^3}$$

$$V_o = 0$$

P.18.5 .

DATA : $R_1 = 10 \text{ K}\Omega = 10 \times 10^3 \Omega$
 $R_2 = 40 \text{ K}\Omega = 40 \times 10^3 \Omega$

Gain of non inverting amplifier = $G = ?$

Sol. Using the rel.;

$$G = 1 + \frac{R_2}{R_1}$$

$$= 1 + \frac{40 \times 10^3}{10 \times 10^3}$$

$$= 1 + \frac{40}{10}$$

$$G = 1 + 4 = \boxed{5}$$